

Digital Design and Computer Organisation Laboratory

UE22CS251A


3rd Semester, Academic Year 2023

Name: ASHLESHA.T	SRN: PES1UG22CS118	Section B
-------------------------	---------------------------	---------------------

Week# 2

Program Number: ____1____

TITLE: IMPLEMENT THE GIVEN CIRCUIT

 

Source code:


```
w2cir1.v
1  module and2(p,c,b);
2  input c,b;
3  output p;
4  assign p=c&b;
5  endmodule
6
7  module or2(x,a,p);
8  input a,p;
9  output x;
10 assign x=a|p;
11 endmodule
12
13 module w2cir1(y,a,b,c);
14 input a,b,c;
15 wire p;
16 output y;
17 and2 and_2(p,b,c);
18 or2 or_2(y,a,p);
19 endmodule
```

```
w2cir1_tb.v
1  module w2cir1_tb;
2  reg a,b,c;
3  wire y;
4  w2cir1 cir1_test(y,a,b,c);
5  initial
6  begin
7  a=0;b=0;c=0; #10;
8  a=0;b=0;c=1; #10;
9  a=0;b=1;c=0; #10;
10 a=0;b=1;c=1; #10;
11 a=1;b=0;c=0; #10;
12 a=1;b=0;c=1; #10;
13 a=1;b=1;c=0; #10;
14 a=1;b=1;c=1; #10;
15 a=0;b=0;c=0; #10;
16 end
17 initial
18 begin
19 $monitor($time," a=%b b=%b c=%b y=%b",a,b,c,y);
20 end
21 initial
22 begin
23 $dumpfile("w2_test.vcd");
24 $dumpvars(0,w2cir1_tb);
25 end
26 endmodule
```

VVP OUTPUT:

```
PS C:\iverilog\bin> iverilog -o test w2cir1.v w2cir1_tb.v
PS C:\iverilog\bin> vvp test
VCD info: dumpfile w2_test.vcd opened for output.
      0 a=0 b=0 c=0 y=0
     10 a=0 b=0 c=1 y=0
     20 a=0 b=1 c=0 y=0
     30 a=0 b=1 c=1 y=1
     40 a=1 b=0 c=0 y=1
     50 a=1 b=0 c=1 y=1
     60 a=1 b=1 c=0 y=1
     70 a=1 b=1 c=1 y=1
     80 a=0 b=0 c=0 y=0
```

GTK WAVE:

 


Name: ASHLESHA.T	SRN: PES1UG22CS118	Section B
-------------------------	---------------------------	-------------------------

Week# 2

Program Number: ____2____

TITLE :

 

$$Y = [A2 \text{ OR } (C2 \text{ AND } B2)] \text{ OR } (B2 \text{ AND } A2)$$

SOURCE CODE:

```

w2cir2.v
1  module and2(p,c,b);
2  input c,b;
3  output p;
4  assign p=c&b;
5  endmodule
6
7  module or2(x,a,p);
8  input a,p;
9  output x;
10 assign x=a|p;
11 endmodule
12
13 module circuit_2(x,a,c,b);
14 input a,c,b;
15 output x;
16 wire p;
17 and2 and2_1(p,b,c);
18 or2 or2_1(x,a,p);
19 endmodule
20
21 module w2cir1(y,a,b,c);
22 input a,b,c;
23 output y;
24 wire x;
25 circuit_2 circuit2_1(x,a,b,c);
26 circuit_2 circuit2_2(y,x,b,a);
27 endmodule
  
```

```

w2cir1_tb.v
1  module w2cir1_tb;
2  reg a,b,c;
3  wire y;
4  w2cir1 cir1_test(y,a,b,c);
5  initial
6  begin
7    a=0;b=0;c=0; #10;
8    a=0;b=0;c=1; #10;
9    a=0;b=1;c=0; #10;
10   a=0;b=1;c=1; #10;
11   a=1;b=0;c=0; #10;
12   a=1;b=0;c=1; #10;
13   a=1;b=1;c=0; #10;
14   a=1;b=1;c=1; #10;
15   a=0;b=0;c=0; #10;
16  end
17  initial
18  begin
19    $monitor($time," a=%b b=%b c=%b y=%b",a,b,c,y);
20  end
21  initial
22  begin
23    $dumpfile("w2_test.vcd");
24    $dumpvars(0,w2cir1_tb);
25  end
26  endmodule
  
```

```
PS C:\iverilog\bin> iverilog -o test w2cir2.v w2cir1_tb.v
PS C:\iverilog\bin> vvp test
VCD info: dumpfile w2_test.vcd opened for output.
      0 a=0 b=0 c=0 y=0
     10 a=0 b=0 c=1 y=0
     20 a=0 b=1 c=0 y=0
     30 a=0 b=1 c=1 y=1
     40 a=1 b=0 c=0 y=1
     50 a=1 b=0 c=1 y=1
     60 a=1 b=1 c=0 y=1
     70 a=1 b=1 c=1 y=1
     80 a=0 b=0 c=0 y=0
PS C:\iverilog\bin> █
```

GTK WAVE:

